

**B.Tech Degree III Semester Examination November 2005****CS/EC/EB/EI/EE 304 DIGITAL ELECTRONICS**

(2002 Admissions onwards)

Time : 3 Hours

Max. Marks:100

- I a) Perform the following conversions:
- i)  $(101)_8 = ( )_{16}$
- ii)  $(101)_{16} = ( )_2$
- iii)  $(101)_{10}$  to equivalent BCD
- iv)  $(101)_2$  to equivalent Graycode (12)
- b) Minimize the given function using Boolean theorems.  
 $F(A, B, C) = A + ABC + \bar{A}B + \bar{A}BC$  (8)
- OR**
- II a) Design a circuit to count the number of ones in a 3 bit number. (10)
- b) Minimize the given function using Quine McClusky:  
 $F(A, B, C) = \sum m(3, 5, 6) + d(1, 7)$  (10)
- OR**
- III a) Given D flip flops, design a 3 bit synchronous up down counter. (12)
- b) With waveforms explain the working of a 4 bit Ring counter. (8)
- OR**
- IV a) Draw and explain circuit of an asynchronous counter which counts from 1 to 5. Use T flip flops and NAND gates. (10)
- b) Draw the circuit of a master slave JK flip flop and explain. (10)
- OR**
- V a) Draw and explain one method of improving the speed of addition. (10)
- b) Draw the circuit of a mono stable multi vibrator and explain with the help of necessary waveforms. (10)
- OR**
- VI a) Design a circuit for a full subtractor. (8)
- b) Draw a circuit to perform binary multiplication and explain with examples. (12)
- OR**
- VII a) Explain the different classifications of memories. (12)
- b) What is PLA? Explain. (8)
- OR**
- VIII a) Differentiate between:
- i) PLA and PAL
- ii) RAM and ROM (8)
- b) Explain how a RAM cell stores data. (12)
- OR**
- IX a) Define the following terms:
- i) Sinking current
- ii) Noise margin
- iii) Totem pole output
- iv) Fan out (12)
- b) Draw the circuit of a TTL inverter and explain. (8)
- OR**
- X a) Explain the following:
- i) Tristate logic
- ii) Propagation delay (6)
- b) Draw the input and output voltage profiles of a TTL gate and explain. (8)
- c) Draw and explain the circuit of an RTL, NOR gate. (6)

\*\*\*

